

Section 14


Shift Registers

Finite State Machines (FSM)

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Shift Registers

 - Shift Registers are a useful part of digital design in:
 - Serial to Parallel Conversion.
 - Pattern Detection
 - Element Extraction
 - Etc.



Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Shift Registers – Serial to Parallel

- The data input stream is scalar (1-bit) the data output stream is an 8-bit vector.
- The data output clock will be 1/8th the speed of the input clock.

```
module sertopar (DOUT,DIN,INCLK,OUTCLK,RESET);
input DIN, INCLK, OUTCLK, RESET;
output [7:0] DOUT;
reg [7:0] DOUT, shftreg;

always @(posedge INCLK or posedge RESET) begin
  if (RESET) shftreg <= 0;
  else begin
    shftreg[7] <= shftreg[6];
    shftreg[6] <= shftreg[5];
    shftreg[5] <= shftreg[4];
    shftreg[4] <= shftreg[3];
    shftreg[3] <= shftreg[2];
    shftreg[2] <= shftreg[1];
    shftreg[1] <= shftreg[0];
    shftreg[0] <= DIN;
  end
end

always @(posedge OUTCLK or posedge RESET) begin
  if (RESET) DOUT <= 0;
  else DOUT <= shftreg;
end
endmodule
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Shift Registers – Serial to Parallel

- Alternate Form for Shift Register.
 - Move blocks when shifting rather than bits.

```
module sertopar (DOUT,DIN,INCLK,OUTCLK,RESET);  
  
    input DIN, INCLK, OUTCLK, RESET;  
    output [7:0] DOUT;  
  
    reg [7:0] DOUT, shftreg;  
  
    always @(posedge INCLK or posedge RESET) begin  
        if (RESET) shftreg <= 0;  
        else begin  
            shftreg[7:1] <= shftreg[6:0];  
            shftreg[0] <= DIN;  
        end  
    end  
    always @(posedge OUTCLK or posedge RESET) begin  
        if (RESET) DOUT <= 0;  
        else DOUT <= shftreg;  
    end  
  
endmodule
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Shift Register - Serial to Parallel

- Testbench
 - Why is OUTCLK delayed by 1ms?

```
'timescale 1ms/10us
module tb;

reg DIN, INCLK, OUTCLK, RESET;
integer i;
wire [7:0] DOUT;

sertopar u1 (DOUT,DIN,INCLK,OUTCLK,RESET);

always #10 INCLK = ~INCLK;

initial begin
#1;
forever #80 OUTCLK = ~OUTCLK;
end

initial begin
{DIN, INCLK, OUTCLK, RESET} = 0;
#1 RESET = 1;
#2 RESET = 0;
for (i = 0; i < 2048; i = i + 1) begin
@(negedge INCLK) DIN = $random;
end
#100 $finish;
end
endmodule
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Shift Registers – Pattern Detection

- PATTERNMATCH will go high whenever the value of the shift register matches the PATTERN parameter.
 - Use conditional constructs to find patterns in Data.

```
module pattern (PATTERNMATCH,DIN,CLK,RESET);  
  
    input DIN, CLK, RESET;  
    output PATTERNMATCH;  
  
    parameter PATTERN = 8'b11001100;  
  
    reg [7:0] shftreg;  
  
    assign PATTERNMATCH = (PATTERN == shftreg) ? 1 : 0;  
  
    always @ (posedge CLK or posedge RESET) begin  
        if (RESET) begin  
            shftreg <= 0;  
        end  
        else begin  
            shftreg[7:1] <= shftreg[6:0];  
            shftreg[0] <= DIN;  
        end  
    end  
endmodule
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Shift Registers – Pattern Detection

- Testbench

```
'timescale 1ms/10us
module tb;
reg DIN, CLK, RESET;
integer i;

pattern u1 (PATTERNMATCH,DIN,CLK,RESET);


always #10 CLK = ~CLK;

initial begin
{DIN, CLK, RESET} = 0;
#1 RESET = 1;
#2 RESET = 0;
repeat (2) begin
    for (i = 0; i < 64; i = i + 1) begin
        @(negedge CLK) DIN = $random;
    end
    #100;
    @(negedge CLK) DIN = 1;
    @(negedge CLK);
    @(negedge CLK) DIN = 0;
    @(negedge CLK);
    @(negedge CLK) DIN = 1;
    @(negedge CLK);
    @(negedge CLK) DIN = 0;
    @(negedge CLK);
end
#100 $finish;
end
endmodule
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Shift Registers – Element Extraction

 - Data can be embedded in synchronization code.
- For Example 8 bit data embedded in 5 sync bits of leading data, and 4 sync bits of trailing data.
 - Data stream :



```
module elementextract (DOUT,DIN,CLK,RESET);  
  
input DIN, CLK, RESET;  
output [7:0] DOUT;  
  
reg [16:0]      shftreg;  
reg [7:0]       DOUT;  
  
parameter leadingsync = 5'b10110;  
parameter trailingsync = 4'b1001;  
  
always @ (posedge CLK or posedge RESET) begin  
    if (RESET) begin  
        DOUT <= 0;  
        shftreg <= 0;  
    end  
    else begin  
        shftreg[16:1] <= shftreg [15:0];  
        shftreg[0] <= DIN;  
        if ((shftreg[16:12] == leadingsync) & (shftreg[3:0] == trailingsync))  
            DOUT = shftreg[11:4];  
        else  
            DOUT = 'bz;  
    end  
end  
endmodule
```

Shift Registers – Element Extraction

- Testbench

```
`timescale 1ms/10us
module tb;

reg CLK, RESET, DIN;
integer i;
wire [7:0] DOUT;

// leadingsync = 5'b10110; trailingsync = 4'b1001;

elementextract u1 (DOUT,DIN,CLK,RESET);

always #10 CLK = ~CLK;


initial begin
{RESET,CLK} = 0;
#2 RESET = 1;
#1 RESET = 0;
repeat (40) @(negedge CLK) DIN = $random;
repeat (10) begin
@(negedge CLK) DIN = 1;
@(negedge CLK) DIN = 0;
@(negedge CLK) DIN = 1;
@(negedge CLK);
@(negedge CLK) DIN = 0;
repeat (8) @(negedge CLK) DIN = $random;
@(negedge CLK) DIN = 1;
@(negedge CLK) DIN = 0;
@(negedge CLK);
@(negedge CLK) DIN = 1;
end // repeat (10)
#100 $stop;
end

endmodule
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Finite State Machines

 
- Finite State Machine Elements:
 - A state register is defined
 - States defined as Parameters.
 - Not necessary, but much easier to read and program.
 - State changes handled in case statements.



```
module explicit_fsm (OUT, CLK, IN, RESET);
  input CLK, IN, RESET;
  output OUT;
  reg STATE, OUT;
  parameter state0 = 0;
  parameter state1 = 1;
  always @(posedge CLK or posedge RESET)
    if (RESET)
      {STATE,OUT} <= 2'b00;
    else
      case (STATE)
        state0: begin
          OUT <= 0;
          if (~IN) STATE <= 0;
          else STATE <= 1;
        end
        state1: begin
          OUT <= IN;
          STATE <= 0;
        end
      default: {STATE,OUT} <= 2'b00;
    endcase
  endmodule
```

Finite State Machines – Example 1

- State Diagram

 

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Finite State Machines – Example 1

RTL Code

```
module fsm (OUT1,OUT2,CLK,IN1,IN2,RESET);

input CLK, RESET, IN1, IN2;
output OUT1,OUT2;
reg OUT1, OUT2;
reg [1:0] current_state, next_state;

parameter idle = 0;
parameter state1 = 1;
parameter state2 = 2;

always @ (posedge CLK or posedge RESET)
if (RESET)
    current_state <= idle;
else
    current_state <= next_state;

always @ (current_state or IN1 or IN2)begin
    case(current_state)

idle : begin
    OUT2 = 0;
    if (IN1 || IN2) OUT1 = 1;
    else OUT1 = 0;
    if(IN1 == 1) next_state = state1;
    else next_state = idle;
end
state1 : begin
    OUT2 = 1; OUT1 = 0;
    if(IN2 == 1) next_state = state2;
    else next_state = idle;
end
state2 : begin
    OUT2 = 0; OUT1 = 0;
    next_state = idle;
end
default : begin
    OUT1 = 1'b1; OUT2 = 1'b1;
    next_state = idle;
end
endcase
end

endmodule
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Some designers will explicitly encode their state variables to avoid glitches (i.e. Gray code or One-Hot). Others will add synthesis constraints to force encoding, such as:


```
#Synopsys Design Compiler FSM Encoding Constraint
set_fsm_encoding_style one_hot
```

At synthesis, this would change the state encoding to:

```
idle = 3'b001;
state1 = 3'b010;
state2 = 3'b100;
```

Finite State Machine – Example 2

 
- Traffic Light Controller
 - Simple intersection light with East-West and North-South control.



Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Finite State Machine – Example 2

 - Default (NSG_EWR) is North-South light green, East-West light red.
- Light will change from green to yellow after 30 seconds.
- Light will remain yellow for 5 seconds.
- Both lights will be red for two seconds.
- External timers will be controlled by the State Machine.



Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Finite State Machine – Example 2

```
module trafficlight (NSGREEN, NSYELLOW, NSRED, EWGREEN,
                     EWYELLOW, EWRED, TIMER30START,
                     TIMER5START, TIMER2START, CLK, RESET,
                     TIMER30, TIMER5, TIMER2);

    input CLK, RESET, TIMER30, TIMER5, TIMER2;
    output NSGREEN, NSYELLOW, NSRED, EWGREEN, EWYELLOW,
           EWRED, TIMER30START, TIMER5START, TIMER2START;

    reg NSGREEN, NSYELLOW, NSRED, EWGREEN, EWYELLOW,
         EWRED, TIMER30START, TIMER5START, TIMER2START;

    reg [2:0] STATE, NEXTSTATE;

    parameter NSG_EWR = 0;
    parameter NSY_EWR = 1;
    parameter NSR_EWR = 2;
    parameter EWG_NS = 3;
    parameter EWY_NS = 4;
    parameter EWR_NS = 5;

    always @(posedge CLK or posedge RESET) begin
        if (RESET) STATE <= state0;
        else STATE <= NEXTSTATE;
    end
```

```
always @((TIMER30, TIMER5, TIMER2, STATE) begin
    case (STATE)
        NSG_EWR : begin
            NSGREEN = 1;
            NSYELLOW = 0;
            NSRED = 0;
            EWGREEN = 0;
            EWYELLOW = 0;
            EWRED = 1;
            TIMER30START = 1;
            TIMER5START = 0;
            TIMER2START = 0;
            if (TIMER30 == 1) NEXTSTATE = NSY_EWR;
            else NEXTSTATE = STATE;
        end
        NSY_EWR : begin
            NSGREEN = 0;
            NSYELLOW = 1;
            NSRED = 0;
            EWGREEN = 0;
            EWYELLOW = 0;
            EWRED = 1;
            TIMER30START = 0;
            TIMER5START = 1;
            TIMER2START = 0;
            if (TIMER5 == 1) NEXTSTATE = NSR_EWR;
            else NEXTSTATE = STATE;
        end
        NSR_EWR : begin ...
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Finite State Machine – Example 2

```
NSR_EWR : begin
    NSGREEN = 0;
    NSYELLOW = 0;
    NSRED = 1;
    EWGREEN = 0;
    EWYELLOW = 0;
    EWRED = 1;
    TIMER30START = 0;
    TIMER5START = 0;
    TIMER2START = 1;
    if (TIMER2 == 1) NEXTSTATE = EWG_NSR;
    else NEXTSTATE = STATE; end
EWG_NSR : begin
    NSGREEN = 0;
    NSYELLOW = 0;
    NSRED = 1;
    EWGREEN = 1;
    EWYELLOW = 0;
    EWRED = 0;
    TIMER30START = 1;
    TIMER5START = 0;
    TIMER2START = 0;
    if (TIMER30 == 1) NEXTSTATE = EWY_NSR;
    else NEXTSTATE = STATE; end
EWY_NSR : begin
    NSGREEN = 0;
    NSYELLOW = 0;
    NSRED = 1;
    EWGREEN = 0;
    EWYELLOW = 1;
    EWRED = 0;
    TIMER30START = 0;
    TIMER5START = 1;
    TIMER2START = 0;
    if (TIMERS == 1) NEXTSTATE = EWR_NSR;
    else NEXTSTATE = STATE; end
```

```
EWR_NSR : begin
    NSGREEN = 0;
    NSYELLOW = 0;
    NSRED = 1;
    EWGREEN = 0;
    EWYELLOW = 0;
    EWRED = 1;
    TIMER30START = 0;
    TIMER5START = 0;
    TIMER2START = 1;
    if (TIMER2 == 1) NEXTSTATE = NSG_EWR;
    else NEXTSTATE = STATE; end
default : begin
    NSGREEN = 1;
    NSYELLOW = 0;
    NSRED = 0;
    EWGREEN = 0;
    EWYELLOW = 0;
    EWRED = 1;
    TIMER30START = 1;
    TIMER5START = 0;
    TIMER2START = 0;
    NEXTSTATE = NSG_EWR;
end
endcase
end
endmodule
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Finite State Machine – Example 2

- Synthesis tool should recognize the state machine.

```
=====
*          HDL Synthesis
=====
Synthesizing Unit <trafficlight>.
Related source file is trafficlight.v.
Found finite state machine <FSM_0>
for signal <STATE>.
-----
| States           | 6
|
| Transitions     | 12
|
| Inputs          | 3
|
| Outputs         | 9
|
| Reset type      | asynchronous
|
| Encoding        | automatic
|
| State register  | d flip-flops
|
-----
Summary:
inferred 1 Finite State Machine(s).
Unit <trafficlight> synthesized.
=====
```

Review

- What uses to Shift Registers have?
- How do you shift data through a Shift Register?
- Are FSMs synthesizable?
- What is the recommended was to declare your state variables?

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS