

Section 5

Gate Level Modeling

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Verilog Primitives

- Verilog primitives are basic gates built into the Verilog language.
- Reference designators are not required for Verilog primitives.
- Some of the “built-in” primitives:

Gate Type	Functionality
and	Logical AND
or	Logical OR
not	Inverter
bufif1	Conditional buffer (enabled high);
...	...


Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Verilog has many “built-in” gate level primitives:

and
nand
or
nor
xor
xnor
buf
not
bufif1
bufif0
notif1
notif0

Structural (Gate Level) Modeling

 - A structural model is equivalent to a schematic diagram.
- A structural model is created from existing components including Verilog “built-in” primitives, pre-defined modules, or user defined primitives.









```
module rs_lat (y, yb, r, s);
input r, s;
output y, yb;

nor u1 (y, r, yb);
nor u2 (yb, s, y);

endmodule
```

Gate Types – and/or

      

- Verilog has a set of and/or type primitives.
- and/or gates have multiple scalar inputs and one scalar output.

```
module andorexmp (andout, nandout, orout,  
                 norout, xorout, xnorout,  
                 a, b);
```

```
output andout, nandout, orout, norout,  
       xorout, xnorout;
```

```
input a, b;
```

```
and (andout, a, b);  
nand (nandout, a, b);  
or (orout, a, b);  
nor (norout, a, b);  
xor (xorout, a, b);  
xnor (xnorout, a, b);
```

```
endmodule
```

Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

and

or

Truth Tables – and/or

a

<i>and</i>	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

b

a

<i>or</i>	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

b

a

<i>xor</i>	0	1	x	z
0	0	1	x	x
1	1	0	x	x
x	x	x	x	x
z	x	x	x	x

b

a

<i>nand</i>	0	1	x	z
0	1	1	1	1
1	1	0	x	x
x	1	x	x	x
z	1	x	x	x

b

a

<i>nor</i>	0	1	x	z
0	1	0	x	x
1	0	0	0	0
x	x	0	x	x
z	x	0	x	x


b

a


<i>xnor</i>	0	1	x	z
0	1	0	x	x
1	0	1	x	x
x	x	x	x	x
z	x	x	x	x

b

Gate Types – buf/not

 

 - Verilog has a buffer (pass-through) primitive, and an inverter primitive.
- buf/not gates have one scalar input and multiple scalar outputs.



```
module bufnotexmp (bufout, notout, in);  
  
    output bufout, notout;  
  
    input in;  
  
    buf (bufout, in);  
    not (notout, in);  
  
endmodule
```

buf

Truth Tables – buf/not

buf

In	Out
1	1
0	0
x	x
z	x


not

In	Out
1	0
0	1
x	x
z	x


Verilog HDL (EE 499/599 CS 499/599) – © 2004 AMIS

Gate Types – conditional buf/not


bufif1

 


bufif0

 

notif1

 

notif0

 

- Verilog has 4 different built in conditional primitives.
- They can only have 3 scalar pins: Input, Output, and Control.
- The output goes to high impedance ('z') when the enable pin is false.

```
module condexmp (bufif1out, bufif0out,
                 notif1out, notif0out,
                 in, ctrl);

    output bufif1out, bufif0out, notif1out, notif0out;
    input in, ctrl;

    bufif1 (bufif1out, in, ctrl);
    bufif0 (bufif0out, in, ctrl);
    notif1 (notif1out, in, ctrl);
    notif0 (notif0out, in, ctrl);

endmodule
```


Truth Tables – Conditional buf/not

		ctrl				
		<i>bufif1</i>	0	1	x	z
in	0	z	0	x	x	
	1	z	1	x	x	
	x	z	x	x	x	
	z	z	x	x	x	


		ctrl				
		<i>bufif0</i>	0	1	x	z
in	0	0	z	x	x	
	1	1	z	x	x	
	x	x	z	x	x	
	z	x	z	x	x	

		ctrl				
		<i>notif1</i>	0	1	x	z
in	0	z	1	x	x	
	1	z	0	x	x	
	x	z	x	x	x	
	z	z	x	x	x	

		ctrl				
		<i>notif0</i>	0	1	x	z
in	0	1	z	x	x	
	1	0	z	x	x	
	x	x	z	x	x	
	z	x	z	x	x	

Primitive Pins

- Pins are expandable for Verilog primitives, except for conditional primitives (`bufif1`, `notif1`, etc.).
 - Multiple outputs, one input allowed for *not* and *buf*.
 - Multiple inputs, one output allowed for *and/or* primitives.
- Syntax:
 - Multiple inputs: `<and/or set> <ref desg. (optional)> (<output>, <input1>, <input2>, ..., <inputn>);`
 - Multiple outputs: `<not or buf> <ref desg. (optional)> <output1>, <output2> ..., <outputn>, <input>;`

 

Specifying Gate Delays

- You can specify gate delays in Verilog primitives.
- Rise, Fall, and Turn-off Delays
 - Rise ('0' to 'x' or '1')
 - Fall ('1' to 'x' or '0')
 - Turn-off ('1', '0', or 'x' to 'z')

```
bufif0 #(5) u1 (q, a, en);           // Rise=5, Fall=5, Turn-off=5
bufif0 #(5,3) u1 (q, a, en);        // Rise=5, Fall=3, Turn-off=min(5,3)=3
bufif0 #(5,4,3) u1 (q, a, en);      // Rise=5, Fall=4, Turn-off=3
```

Delay specification can only be added to primitives

Gate Delays

- Example: An *and* gate with a rise delay of 1ns and a fall delay of 2ns.

```
module andexamp (out, a, b);  
  
    output out;  
    input a, b;  
  
    and #(1,2) (out, a, b);  
  
endmodule
```




Gate Delays (cont.)

- Verilog allows three delay values to be specified as a triplet using colons (:) as separators. (i.e., (min:typ:max))
- The value used is specified at run time as a command line argument (+mindelays, +typdelays, +maxdelays)

```
bufif0 #(4:5:6) u1 (q, a, en);  
bufif0 #(4:5:6, 2:3:4) u1 (q, a, en);  
bufif0 #(4:5:6, 2:3:4, 1:2:3) u1 (q, a, en);
```

Primitive Instantiation

 

```
module addbit (a, b, ci, sum, co);  
  input a, b, ci;  
  output sum, co;  
  xor #(2) u1 (n1, a, b);  
  xor #(2,1) u2 (sum, n1, ci);  
  and (strong1, weak0) #(1, 1.5) u3 (n2, a, b);  
  and u4 (n3, sum, ci);  
  or u5 (co, n2, n3);  
endmodule
```

Module Instantiation

- A module instantiation must have an instance name
- In positional mapping, the port order is the same as in the module declaration
- In name mapping, no order is required.

```
module add4bits (result, carry, r1, r2, ci);  
...  
  addbit u1 (r1[0], r2[0], ci, result[0], c1);           // positional mapping  
  addbit u2 (.a(r1[1]), .ci(c1), .b(r2[1]), .sum(result[1]), .co(c2)); // named mapping  
  addbit u3 (r1[2], , c2, result[2], c3);             // one port left unconnected  
  addbit u4 (.a(r1[3]), .sum(result[3]), .co(carry)); // named with two unconnected ports  
endmodule
```

Module Instantiation – Array of Instances

- An array of instances can be created using one base instance.
- The port names must be the same throughout the instance array.
- Useful for bussed ports. The instance “value” will match the vector bit in the instance array.

```
module busena (Q, A, EN);  
  input [3:0] A;  
  input EN;  
  output [3:0] Q;  
  wire [3:0] A, Q; wire EN;  
  bufif0 u[3:0] (Q, A, EN);  
endmodule
```


=

```
module busena (Q, A, EN);  
  input [3:0] A;  
  input EN;  
  output [3:0] Q;  
  wire [3:0] A, Q; wire EN;  
  bufif0 u3 (Q[3], A[3], EN[3]);  
  bufif0 u2 (Q[2], A[2], EN[2]);  
  bufif0 u1 (Q[1], A[1], EN[1]);  
  bufif0 u0 (Q[0], A[0], EN[0]);  
endmodule
```


Conflict Resolution

- There are 8 signal strengths in Verilog
 - supply, strong, pull, large, weak, medium, small, highz
- Supply is the strongest and highz is the weakest.
- Use the %v format specifier to view signal strength.
 - \$monitor (“output = %v”, signal);
 
```
bufif1 (strong0, weak1) a (out1, a, b);  
bufif1 (pull0, strong1) b (out2, c, d);
```



a output	b output	output
strong1	strong0	strongX
pull0	weak1	pull0
pull0	strong0	strong0

See Appendix A of Verilog HDL by
Palnitkar book for more details

Review

- Which primitives allow multiple inputs but only one output?
 - Which primitives allow only two inputs and one output?
 - Which primitives allow multiple outputs but only one input?
 - How do you model path delays? Are path delays synthesizable?
 - How are signal strength declarations useful in Verilog?
-